

Fast, low-noise JFET amp is stable over temperature

[Shyam Sunder Tiwari](#) - August 03, 2015

While JFETs are excellent devices for low-cost high-input impedance amplifiers, they do suffer from temperature-dependent gain drift. This problem can be ameliorated by setting the drain current to the zero-drift operating point over the -55°C to 125°C temperature range.

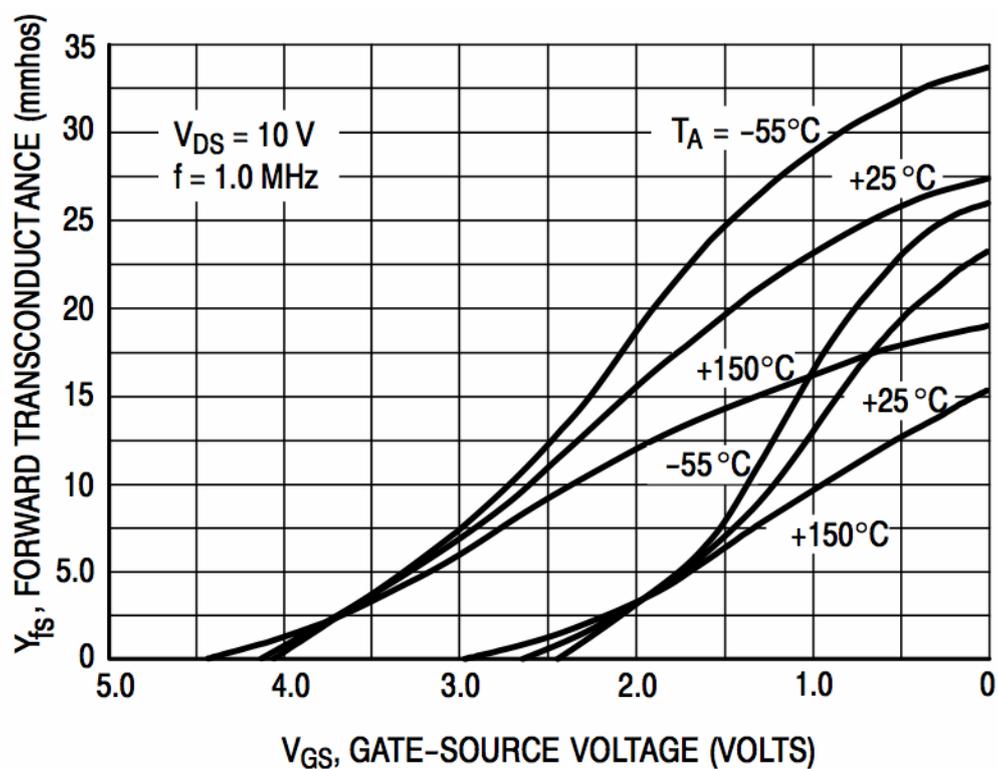


Figure 1 Transconductance curve families over temperature for J310 & J309 JFETs (OnSemi)

Various JFETs have been tested for this Design Idea circuit: Sony 2SK152-2, Interfet IFN152, and Siliconix/Vishay/OnSemi [J309](#), as they have high gain and a low gate leakage current of about 100pA. These JFETs are well suited to 1M Ω - to 1G Ω -input impedance amplifier design. The circuit works well to over 100MHz.

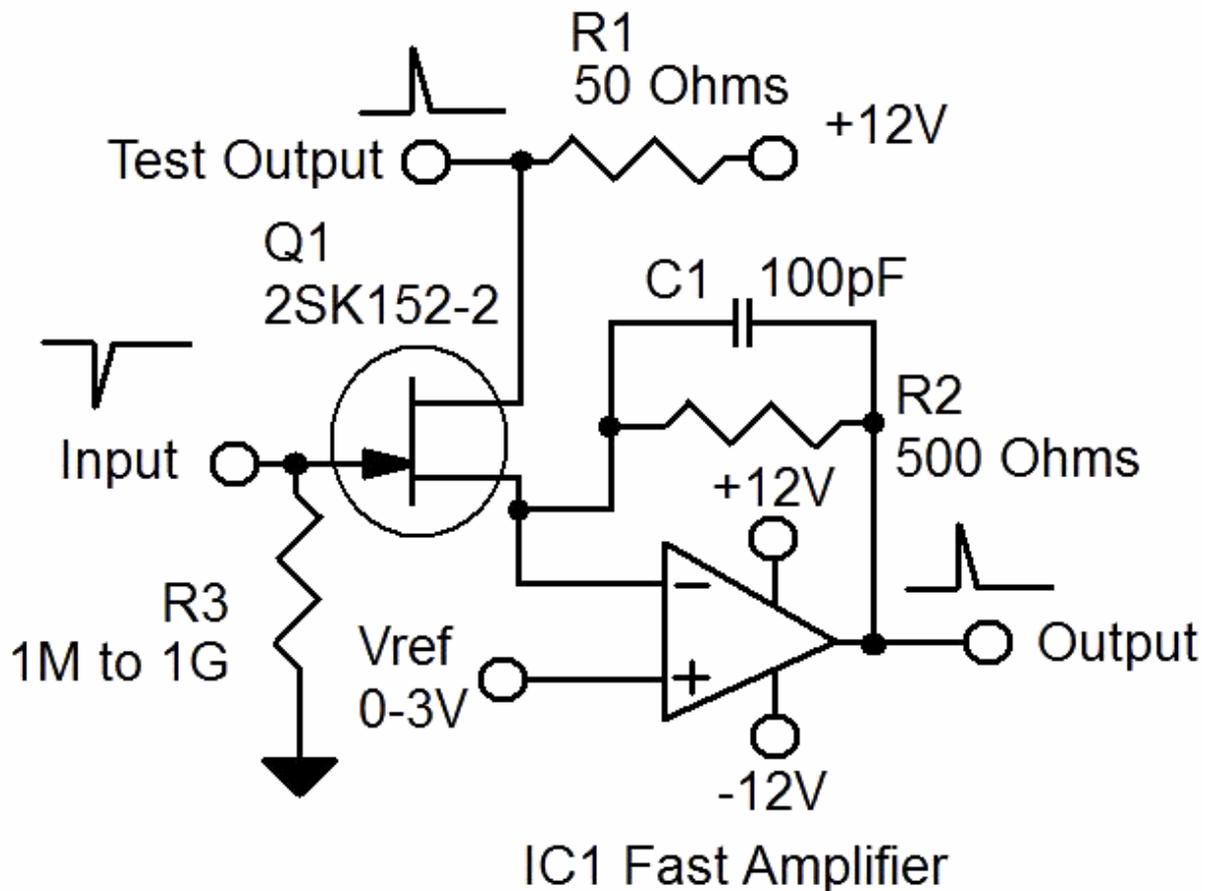


Figure 2 Very wide temperature range, gain-stable, fast JFET high-impedance amplifier

One advantage of the circuit comes from its large operating temperature range (-55°C to 125°C for the JFET). IC1 can be kept at room temperature, linked by a few feet of PTFE coax for example, for temperature isolation. Thus the JFET can be mounted in a very cool environment for lowest noise, which was a primary objective of the design. ✘

The input signal to JFET Q1 is fed to its gate, which is biased to ground through R3 (which could be a lower value in the case of a current-source input).

The JFET's source is biased through the inverting current-to-voltage stage based on IC1. V_{ref} , which controls the quiescent V_{GS} , is set between 0V & 3V for most JFETs to set the drain current at the zero-drift midpoint, which also gives a large dynamic range for the input signal. By adjusting V_{ref} , we can bring Q1's operating current to about 7mA-10mA, which is close to the zero-drift point. The operating current has to be separately analyzed for each JFET to be set properly. For the 2SK152-2, it was found to be 7.5mA \pm 1mA for the 1,000 JFETs I have tested.

IC1 is a fast CFA (current-feedback amplifier): Analog Devices' AD812 at $\pm 12V$ to $\pm 15V$, and AD8009 at $\pm 5V$, have been used successfully. The feedback resistor R2 can be from 500 Ω to 5k Ω , in parallel with C1 of 100pF to avoid oscillations and overshoot. Remember that the output of the amplifier has a voltage offset due to the biased input stage and hence is best suited to AC or pulsed signals. A risetime of 10ns to 100ns is feasible with the proper R2/C1 combination. CFAs are

operated within a gain range of 2-10, set by resistor R2; at much higher gains, the amplifier starts oscillating.



R1 provides a test output to measure the current through the JFET. It also generates a fast 50Ω output which can be directly connected to an oscilloscope. Both output signals are inverted compared to the input signal - typically $\pm 100\text{mV}$. For DC-biased signals, a coupling capacitor of about 1nF-10nF can be used in front of the gate.

Also see:

- [A guide to using FETS for sensor applications, Part 1](#)
- [Condenser microphone uses dc-coupled impedance converter](#)
- [Product How-to: LSK489 Application Note](#)
- [Simple circuit lets you characterize JFETs](#)
- [Op amps make JFET circuits repeatable](#)