

Application Note AN4102

A Fairchild Power Switch based SMPS for Color Television Receivers

Introduction

A switched mode power supply (SMPS) typically consists of a power transformer, secondary side rectifier diodes, a switching semiconductor device, a control IC, and peripheral circuits. Besides its basic function of supplying power to the load on the secondary side, an SMPS may have to perform other, special functions, depending on the system. For example, an SMPS for a color television receiver must minimize the effect of switching noise on the screen and reduce power consumption in standby. If the level of integration of the switching circuitry is not high enough, then additional, separate circuits will be required to accommodate all functions; these additional components raise the overall SMPS cost and not uncommonly reduce reliability. The highly integrated Fairchild Power Switch (FPS) combines a high power MOSFET and control IC into one package and, moreover, enhances IC functionality. It includes protective functions, thereby minimizing the number of additional components needed in an SMPS. Fairchild Power Switch (FPS) is widely used in the power circuits of a variety of equipment, such as color TVs, printers, PCs, monitors, and, of course, battery chargers and ac adapters. The KA3S-series Fairchild Power Switch (FPS) series was first introduced for color TVs; the SMPS described in this application note uses a KA5Q-series Fairchild Power Switch (FPS). KA5Q-series Fairchild Power Switch (FPS) incorporates enhanced protection functions and has a much reduced power consumption in standby mode.

The most frequently used power circuits in household appliances are the flyback converter and the forward converter, both of which use the pulse width modulation (PWM) control method for fixed frequency switching. However, a general purpose PWM based SMPS cannot be used for a monitor or color TV, because the SMPS's switching noise would seriously affect the display quality. The switching noise would appear in the form of picture noise. To significantly reduce the effect of switching noise on the screen a power supply for a monitor has to be able to synchronize its switching frequency to an external signal, typically the monitor's horizontal sync flyback signal. Such a sync technique cannot be used in color TVs, however, since, unlike monitors, a color TV's horizontal deflection frequency is too low. Instead, an SMPS for a color TV makes use of the so called quasi resonant technique. In this technique a

capacitor is added between the MOSFET drain and source, which lowers both the rising slope of the voltage V_{ds} between the MOSFET's drain and source and the falling slope of the reverse voltage across the secondary side rectifier diodes when the MOSFET turns off. The shallower slopes reduce the dV/dt switching noise and switching loss, because the MOSFET turns on when V_{ds} is at a minimum or zero. To comply with regulatory trends aimed at reducing standby power consumption, KA5Q-series Fairchild Power Switch (FPS) features a built in burst mode. Burst mode operation make it possible to reduce output voltages in standby to almost half those of the normal on mode. This can reduce standby input power demand to under 3W at 230Vac or, if few peripheral components are added, to possibly even 1.5W. Moreover, as implemented in the KA5Q-series, burst mode operation causes no audible noise and requires almost no additional components. To reduce losses further, KA5Q-series Fairchild Power Switch (FPS) has lower IC start up and operating currents than the KA3S-series, and quasi resonant operation can continue even in burst mode. Also, the KA5Q-series can perform primary side regulation using a built in error amplifier, which replaces the secondary side error amp and eliminates its peripheral circuits. Overall, the KA5Q-series incorporates five protection features to increase SMPS reliability:

- Pulse by pulse over current protection.
- Over voltage protection.
- Over load protection.
- Thermal protection.
- Over current latch.

This application note contains working design example (Section 8) of an SMPS for use with color TVs or other high power applications. It is a universal input supply adaptable to ac input voltages world wide, and uses the Fairchild Power Switch (FPS)'s burst mode capability to achieve very low standby power consumption: less than 2W at 230Vac. The SMPS features variable frequency, quasi resonant switching; current mode control; built in secondary side regulation; and an array of built in protection features, including pulse by pulse over current protection and shutdown, over voltage protection with auto restart, overload protection with auto restart, and thermal shutdown.

1. Quasi resonant Operation

When a hard switched SMPS is used for a color TV, the MOSFET generates a very high frequency current spike at turn on, and this spike shows up as noise on the screen. Also, because the MOSFET's output capacitance, C_{oss} is small, a fast MOSFET turn off abruptly increases its drain to source voltage V_{ds} at a high dV/dt . This generates a voltage spike that produces common mode noise on the secondary side, which again results in on screen noise. Figure 1 shows a flyback converter that uses the quasi resonant technique. L_m is the transformer's primary side magnetizing inductance, and D1 is the MOSFET body diode. Neither the inductor nor the diode is a physically separate component. They are integral and implicit to the transformer and MOSFET, respectively, and are shown in Figure 1 for explanatory purposes. Current I_d , that flows to the MOSFET increases at a constant rate when the MOSFET is on.

 


Figure 1. Simplified diagram of a flyback converter using the quasi resonant technique.

The MOSFET turns off when I_d reaches the peak value (I_p in Figure 2) set by the control circuit, at which time the energy stored in the transformer in the form of flux charges capacitor C_r connected between the MOSFET's drain and source. This raises V_{ds} . The rising slope of V_{ds} increases as I_p increases and characteristic impedance $Z_r = (L_m/C_r)^{1/2}$ decreases. C_r , which is much larger than the MOSFET's output capacitance C_{oss} , controls dV/dt when the MOSFET turns on and off, reducing it from what it would be otherwise. The charging of C_r continues until the secondary side rectifier diode D2 turns on, after which the transformer delivers current to the output. D2 is on for an interval proportional to I_p , during which $V_{ds} = V_{in} + nV_o$, (Figure 2).

 


Figure 2. Waveforms for the circuit of Figure 1.

After all the energy stored in the transformer is delivered to the secondary side, L_m and C_r resonate and V_{ds} starts to decrease. In the ideal case with no losses, the minimum value for V_{ds} would be $V_{in} - V_o$. The actual value is slightly higher. At minimum V_{ds} the sensing circuit turns on the MOSFET. (See Section 5 for a description of the sensing method.) Because the MOSFET is turned on when V_{ds} is minimum and not zero, the potential stored in C_r discharges as soon as the MOSFET turns on, which generates a large current spike. To reduce this spike, the Fairchild Power Switch (FPS)'s control IC is configured to slow the MOSFET's turn-on. The time required for V_{ds} to reach minimum is $T_R (T_R = \pi \sqrt{L_m C_r})$, a fixed value independent of the input voltage or output current. Varying the switching frequency regulates the output voltage: the lower the switching frequency, the lower the input voltage and the higher the load current.

2. Secondary Side vs. Primary Side Regulation

Secondary side regulation requires an error amplifier and an opto coupler on the secondary side. The amplified error is transferred to the primary side through the opto coupler to control the MOSFET's on time and thereby precisely control the output voltage. The opto coupler also transfers the MCU signal received on the secondary side to the primary side to operate the burst mode. As explained in the following section, the burst mode allows low standby power to be achieved. Therefore, should it be necessary to guarantee a minimum standby power, an error amp and opto coupler would be required on the secondary side and the increased cost these components contribute to the design would have to be accepted. Primary side regulation is a method that regulates secondary side voltage indirectly, by controlling the primary side voltage. In the KA5Q-series Fairchild Power Switch (FPS), the error amp in the control IC senses

(see I_{ds} , Figure 5), but the output voltage V_{o2} remains at 45.8% of its normal mode voltage. When V_{cc} finally drops to 11V (45.8% of 24V, its normal mode level), the burst mode controller starts and V_{cc} and V_{o2} increase. When V_{cc} rises to 12V, the MOSFET stops switching and the above operations repeat.

 


Figure 5. Abnormal burst mode operation in an improper design allowing V_{o2} to decrease faster than V_{cc} .

This kind of operation, where V_{o2} decreases faster than V_{cc} extends the switching period and increases the switching loss. To prevent these effects, increase the value of the output rectifier capacitance (see, e.g., the circuit of Section 8 and Table 1, the parts list for that circuit).

4. Feedback Circuit Design

When secondary side regulation is used, the output voltage is determined by comparing the voltage to be controlled, V_{o1} , to the reference in the error amp. In this example it is 2.5 V for an LM431. As shown in Figure 3, when the MCU picture on signal goes high, Q1 turns on and the diode in its collector turns off. Thus, R_{24} and R_{25} around the error amp are determined as follows

$$2.5 = \frac{R_{24}}{R_{24} + R_{25}} V_1$$

$$\therefore R_{25} = \frac{V_1 - 2.5}{2.5} R_{24}$$

In standby mode, however, with the picture on signal low, Q1 is off and the diode is on. Now R_{24} , R_{25} , and R_{26}

determine the output voltage, which is calculated as follows:

$$2.5 = \frac{R_{24} // R_{26}}{R_{25} + R_{24} // R_{26}} V'_1 + \frac{R_{25} // R_{24}}{R_{26} + R_{25} // R_{24}} (V'_2 - 0.7)$$

$$\therefore R_{26} = \frac{R_{25} R_{24} (V'_2 - 0.7 - 2.5)}{2.5 (R_{25} + R_{24}) - V'_1 R_{24}}$$

where, V_1 , and V_2 are the normal mode output voltages, V_{o1} and V_{o2} ; an V'_1 and V'_2 are the desired control loop values for V_{o1} and V_{o2} in standby (45.8% of their normal mode values). This value is set since the Fairchild Power Switch (FPS) regulates its V_{cc} voltage to 11V in standby mode and V_{cc} is normally set to 24V in normal mode.

4.1. Transformer turns ratio

If V_{o2} drops to V'_2 , before V_{cc} drops to 11V in standby mode, the error amp starts to feed back. If V'_2 is too low, the MCU could be reset. Therefore, select V'_2 such that the linear regulator (7805) can properly maintain the output. This means the turns ratio should be selected such that $(11 / V_{cc}) > (V'_2 / V_2)$. In other words, the transformer should be designed so that V_{o2} is maintained slightly higher than V'_2 . This allows the error amp output to saturate low, permitting the primary side V_{fb} to remain at ground level.

5. Fairchild Power Switch Sync Pin Circuitry Design

In quasi resonant operation, the voltage level at the Fairchild Power Switch (FPS) Sync pin (pin 5) determines when the MOSFET turns on. This should be when V_{ds} is lowest.

Figure 6 shows the reference voltages, V_{rh} and V_{rf} for both normal and burst mode operation. They are used to detect the time required for the voltage across the MOSFET to reach its minimum. The MOSFET turns on when the Sync pin voltage becomes lower than V_{rf} .

 


Figure 6. Reference voltages for normal and burst mode operation, V_{rh} and V_{rf} .

Figure 7 shows the waveform of V_{sync} in normal mode. The peak value of $V_{sync}(t)$, when divided by R_{15} and R_{16} must be greater than the threshold voltage of the sync pin. In normal mode the threshold voltage is 4.6 V, and in standby mode it is 3.6V. $V_{sync}(t)$ is the voltage across C_{15} . It increases to V_c , which is the maximum voltage of $V_{sync}(t)$ determined by the auxiliary winding voltage and the ratio of R_{15} and R_{16} , after the MOSFET turns off. When the transformer current drops to zero, it drops exponentially as shown in Figure 7.

 


Figure 7. Normal mode waveforms for $V_{sync}(t)$.

The time t_Q that it takes for $V_{sync}(t)$ to drop from V_c to V_{rf} , is calculated as follows:

$$t_Q = \tau \ln \left(1 - \frac{V_{rf}}{V_c} \right)^{-1}$$

$$\text{where } \tau = R_{16} C_{12} \quad V_c = \frac{R_{16}}{R_{15} + R_{16}} V_{cc}$$

When t_{Q1} as calculated from V_{c1} and V_{rf1} equals t_{Q2} as calculated from V_{c2} and V_{rf2} , the following relationship can be derived:

$$\frac{V_{rf1}}{V_{c1}} = \frac{V_{rf2}}{V_{c2}}$$

Therefore, $t_{Q1} = t_{Q2}$ and are independent of t , and t_Q will not change so long as the ratio of V_c to V_{rf} is constant. When the transformer flyback current becomes zero, V_{ds} starts to decrease. The time required for the voltage across the

MOSFET to drop to its minimum value is:

$$t_R = \pi \sqrt{L_m C_r}$$

The equation shows that the time required to drop to minimum voltage is a function of the primary inductance, L_m , and capacitance, C_r , across the MOSFET. This means that t_R is independent of changes in input and output voltage

and does not change once the circuit is set.

 


Figure 8. Stand by mode V_{sync} waveform.

The output voltage in standby drops to 45-50% of its value in normal mode, and so does V_c . Therefore, to guarantee quasi resonant operation in standby mode, t_Q must equal t_R , regardless of the mode. To achieve this, the reference in the Fairchild Power Switch (FPS)'s Sync pin comparator changes with the mode.

6. Protection

6.1 Over voltage protection

Refer to Figure 8. A problem in the feedback loop can be indicated either when switching shuts down or the output voltage is continuing to increase because it is not regulated. In response to increasing output voltage, a KA5Q-series Fairchild Power Switch (FPS) enters latch mode when the sync pin voltage reaches 12V (typ.) The Fairchild Power Switch (FPS) stops, and all output voltages start to drop. When V_{cc} reaches 9V, the Fairchild Power Switch (FPS) unlatches and restarts and V_{cc} again increases. Switching restarts when V_{cc} reaches 15V. This operation is called auto restart. Be careful of the rising slope of $V_{sync}(t)$. Its time constant is $C_{12} \times (R_{15} // R_{16})$. If the time constant is too short, the waveform can oscillate causing an over voltage protection (OVP) malfunction. If V_c , the peak value of $V_{sync}(t)$ approaches the OVP level (12V, typ.) and there are problems in the feedback loop. Output voltage overshoot is reduced but care must be taken so that the OVP does not malfunction due to a slight overshoot, etc. in the output voltage. If V_c is set too low, the Fairchild Power Switch (FPS)'s Primary Side Regulation (PSR) block can start before OVP and regulate V_{cc} . In that case operation continues, but with an abnormally increased output voltage.

6.2 Thermal shutdown

If the ambient temperature is high, or the temperature inside the device becomes too high due to abnormal operation, the junction temperature of the device can become too high. If it exceeds 150°C, the Fairchild Power Switch (FPS) enters latch mode and stops.

6.3 Over current latch

A short circuit in a secondary side rectifier diode or on a transformer pin is equivalent to a leakage inductor of several mH connected to the input bulk capacitor. A large current spike can flow through the MOSFET in the Fairchild Power Switch (FPS), and the MOSFET will be destroyed if the current is not turned off within a few hundred nanoseconds. Although ICs with current mode control generally have over current protection, it may not execute properly due to delays in the IC's internal blocks. Hence, besides using pulse by pulse over current protection to turn off the MOSFET, the Fairchild Power Switch (FPS) also uses an over current latch. This allows the Fairchild Power Switch (FPS) to turn off the MOSFET within 200 ns if the current flow is higher than the over current protection level threshold. The Fairchild Power Switch (FPS) also operates in latch mode to reduce stress on the MOSFET that would result from repeated auto restarts. Once the Fairchild Power Switch (FPS) enters latch mode, the input ac power is cut off. The Fairchild Power Switch (FPS) will unlatch and restart only when Vcc drops below 5V.

6.4 Over load protection (OLP)

Refer to Figure 9, next page. The feedback loop causes the voltage Vfb, on the Fairchild Power Switch (FPS) feedback pin to increase when the output current increases. In the case of a persistent overload condition, Vfb continues to increase because 5mA current source in the Fairchild Power Switch (FPS) charges the compensation capacitor attached to the FB pin. If this voltage reaches 7.5V, the MOSFET stops switching. The delay between Vfb reaching the over current protection level and when the MOSFET stops switching is calculated as follows:

$$t_{\text{delay}} = \frac{(7.5 - 3) \cdot C_{13}}{5 \times 10^{-6}} [\text{sec}]$$

Auto restart begins after overload protection triggers.

7. PCB Layout

 


Figure 9.

A proper PCB layout not only reduces the set EMI, but also minimizes the noises that can produce device malfunction. Cautionary items when designing the PCB layout of the 5Q-series are as follows:

- The space between 2 pin in the 5Q-series and the bulk capacitor (DC link capacitor) - (Ground) terminal should be simple and close as possible. A thick pattern should be used.
(C↔2 in the fig9, very important)
- PCB pattern should be made such that C_r is as close as possible to pin 1,2. If not, pulse like current flow path becomes longer every time the switch turns on, worsening the noise.
(A↔1, B↔2 in the fig9, very important)
- The distance between 2 pin in the 5Q-series and the negative terminal of Vcc capacitor should be close as possible.
(D↔2 in the fig9, very important)
- The distance between 2 pin in 5Q-series and the negative terminal of Vcc capacitor should be close as possible.
(E↔2 in the fig9, important)
- The distance between 2pin in the 5Q-series and the negative terminal of Vfb capacitor should be close as possible.
(F↔2 in the fig9, important)
- The feedback loop PCB pattern should be simple and not be placed close to a comparatively high current flow connection or device. The connection between the ground

of output which is regulated and the ground of secondary error Amp. is simple and close as possible.

(H↔3 in the fig9, very important)

- when the primary side control is used, the transformer Vcc (pin 3) winding must be made so as to result in the best coupling coefficient between it and the most important winding.


 


Figure 10. Operation Waveform.

8. KA5Q Fairchild Power Switch Based SMPS for a Color TV

8.1 Secondary Side Regulation.

 

8.2 Primary Side Regulation

 


Table 1. Parts List for KA5Q based SMPS

Part #	Value	Rating	Note	Part #	Value	Rating	Note
[Resister]				C104	47 μ F	50V	electrolytic
R101	open	1/2W	-	C105	3.9nF	50V	film
R102	NTC	4.7 Ω	-	C106	open	50V	electrolytic
R103	68k Ω	1/2W	-	C107	2.2nF	1000V	film
R104	68k Ω	1/2W	-	C108	560pF	2000V	film
R105	470 Ω	1/4W	-	C109	47nF	50V	film
R106	600 Ω	1/4W	-	C201	1000 μ F	50V	electrolytic
R107	10 Ω	1/4W	-	C202	1000 μ F	50V	electrolytic
R108	open	1/4W	-	C203	22nF	50V	film
R109	open	1/4W	-	C204	open	50V	film
R201	1k Ω	1/4W	-	C205	470pF	1000V	film
R202	short	fuse	-	C206	470pF	1000V	film
R203	1k Ω	1/4W	-	C207	470pF	1000V	film
R204	40k Ω	1/4W	-	C208	1000 μ F	50V	electrolytic
R205	4.7k Ω	1/4W	-	C209	1000 μ F	50V	electrolytic
R206	220k Ω	1/4W	-	C210	1000 μ F	50V	electrolytic
R207	5k Ω	1/4W	-	C211	1000 μ F	50V	electrolytic
R208	5k Ω	1/4W	-	C212	470pF	1000V	film
VR201	30k Ω	box	-	C213	560pF	2000V	film
VR202	20 k Ω	box	-	C214	100 μ F (100W)	200V	electrolytic
[Diodes]				-	220 μ F (150W)	200V	electrolytic
D101	open	ZNR	-	-	330 μ F (200W)	200V	electrolytic
D102	1N4004	400V, 1A	-	-	330 μ F (270W)	200V	electrolytic
D103	1N4937	600V, 1A	-	C215	47 μ F (100W)	200V	electrolytic
D104	short	600V, 1A	-	-	100 μ F (150W)	200V	electrolytic
D105	1N4937	600 V, 1A	-	-	220 μ F (200W)	200V	electrolytic
D106	1N4148	75V, 0.15A	-	-	220 μ F (270W)	200V	electrolytic
D201	1N4148	75V, 0.15A	-	-	-	-	-
D202	D06U20S(100W)	200V, 6A	TO-220F	-	-	-	-
	D06U20S(150W)	200V, 6A	TO-220F	-	-	-	-
	D06U20S(200W)	200V, 10A	TO-220F	-	-	-	-

Table 1. Parts List for KA5Q based SMPS (continued)

Part #	Value	Rating	Note	Part #	Value	Rating	Note
[Diodes]				[Beads]			
D202	D06U20S(270W)	200V,20A	TO-220F	BEAD101	ferrite bead	-	-
D203	D10U60S	600V,10A	TO-220F	BEAD201	ferrite bead	-	-
	D20U60S(270W)	600V,20A	TO-220F	BEAD202	100 μ H	5A	-
	open	-	-	BEAD203	ferrite bead	-	-
	D06U20S	200V,10A	TO-220F	BEAD204	ferrite bead	-	-
	open	-	-	-	-	-	-
	D06U20S	200V,10A	TO-220F	-	-	-	-
	open	-	-	-	-	-	-
[Zener]				[Others]			
ZD101	4.7V	0.5W	-	OPT101	H11A817A	-	Fairchild
	-	-	-	T101	EER3542	KA5Q0765RT	-
				-	EER4042	KA5Q12656RT	-
C101	220nF	275V	box	-	EER4942	KA5Q1265RT	-
C102	220 μ F (100W)	400V	electrolytic	-	EER5354	KA5Q1565RT	-
	330 μ F (150W)	400V	electrolytic	CON201	PWR CONN.	-	-
	470 μ F (200W)	400V	electrolytic	CON202	PWR CONN.	-	-
	560 μ F (270W)	400V	electrolytic	Q201	KA431LZ	-	-
C103	100nF	50V	film	Q202	C945	npn (E.B.C)	-

9. Example Transformer Design for Color TV SMPS

9.1 Define system specifications:

Output power, $P_o = 80W$ (125V,0.56A for B+ and 13V,0.76A)

$$P_{B-OUT} = 70W, P_{13V-OUT} = 10W$$

Input voltage, 85 to 265 V., (universal input), 60Hz

Efficiency $\eta \geq 80\%$

Core = EER3542 ($A_e = 108mm^2$)

9.2. Calculate minimum dc input voltage, V_{inmin} :

The table below shows typical values of V_{inmin} , L_m , F_{smin} for various P_{in} values. The maximum power input is

$$P_{in_max} = \frac{P_o}{\text{efficiency}} = \frac{80W}{0.8} = 100W$$

For 100W P_{in_max} , there are two option for capacitor value; 220uF or 330uF. Here, select the 220uF.

Then, 93V is the minimum dc input voltage.

Pin (W)	Cin [μF]	Vin_min [V]	Lm [μH]	Fs_min [kHz]
80	220	98	700	26.1
			675	27.0
			650	27.9
	330	105	700	28.0
			675	29.0
			650	30.0
100	220	93	600	23.6
			575	24.5
			550	25.6
	330	102	600	25.9
			575	27.0
			550	28.1
130	330	96	500	23.3
			475	24.4
			450	25.7
	470	103	500	25.0
			475	26.3
			450	27.6
150	330	93	400	26.6
			375	28.2
			350	30.0
	470	101	400	26.6
			375	28.2
			350	30.0
180	470	97	350	24.7
			325	26.5
			300	28.5
	560	101	350	25.7
			325	27.5
			300	29.6
200	470	94	325	23.4
			300	25.3
			275	27.4
	560	98	325	24.5
			300	26.4
			275	28.7

Pin (W)	Cin [uF]	Vin_min [V]	Lm [uH]	Fs_min [kHz]
240	560	94	275	23.3
			250	25.5
			225	28.1
240	680	99	275	24.5
			250	26.8
			225	24.5
270	560	91	250	22.0
			200	24.3
			250	23.4
			200	25.9

However, because of voltage drops from the line filter, bridge diode, and NTC (negative thermal coefficient), set Vinmin to 100V to allow for a design margin and convenient calculation.

9.3 Determine turns ratio, $n = N_p/N_s$:

Turns ratio is a factor in determining Dmax, device operating voltage, and device and transformer dissipation.

$$n = \frac{650V + -\sqrt{2}V_{(acmax)} - 120}{V_o}$$

$$n = \frac{650 - \sqrt{2} \times 265 - 120}{125}$$

$$= 1.25$$

where Vo is the output voltage used for B+ (125V) and 120V is the margin voltage. It can be determined by the designer, or the transformer, etc.

9.4 Calculate maximum duty, Dmax:

$$D_{max} = \frac{V_o}{V_{inmin} + nV_o}$$

$$D_{max} = \frac{1.25 \times 125}{93 + 1.25 \times 125} = 0.62$$

9.5 Calculate transformer inductance, Lm:

Fs, is the minimum operating frequency at the condition of maximum load and minimum input voltage. Therefore Fs, should be set around 25-40kHz. Vinmin

condition is calculated as above at operating frequency of any load. From the operating frequency, it is possible to

estimate the device and transformer dissipation. Using Fs = 30kHz we calculate Lm. Fs should be corrected to 30×10^3 in the equation below.

Following this there should be some explanation of the core

gap calculation to give the correct flux density.

$$L_m = \frac{V_{in}^2 \times D_{max}^2}{2P_{in}f_s}$$

$$L_m = \frac{93^2 \times 0.62^2}{2 \times 100 \times 30K} = 554 \mu H$$

Estimated gap length (l_g) is

$$l_g = \frac{N_p^2 \mu_o A_e}{L_m} \times 10^3$$

$$= \frac{63^2 \times 4\pi \times 10^{-7} \times 108 \times 10^{-6}}{620 \times 10^{-6}} \times 10^3$$

$$= 0.868 \text{ mm}$$

Ae is the cross sectional area of the core
 $\mu_o = 4\pi \times 10^{-7}$

9.6 Calculate minimum primary turns, N_{pmin} :

The primary turns count must be made larger than Npmin to prevent the transformer from saturating below the Fairchild Power Switch (FPS) Ipeak specification.

$$N_{pmin} = \frac{V_{inmin} D_{max}}{(dB)(A_e)(F_{smin})}$$

$$N_{pmin} = \frac{93 \times 0.62 \times 10^6}{0.3 \times 108 \times 30K} \approx 59T$$

where dB is the absolute amount of flux density variation in the core.

9.7 Calculate the maximum current, I_{peak} ,

At full load and at minimum V_{in} , I_{peak} must be lower than the I_{peak} specification of the device to be used.

$$I_{peak} = \frac{V_{inmin} D_{max}}{L_m f_{smin}}$$

$$I_{peak} = \frac{93 \times 0.62}{554 \mu H \times 30k} = 3.46A$$


9.8 Determine each output turns count:

- 125V output: $N_{125V} = N_{pmin} / n = 47$ turns
- Volts per turn: $(125V + 1V) / 50$ turns = 2.68V / turn
- 13V output: $(13V + 1V) / 2.68V / \text{turn} = 5.22 = 5$ turns
- V_{cc} winding: $(24V + 1V) / 2.68V / \text{turn} = 9.32 = 9$ turns

9.9 Determine wire diameter

The copper coil's current capability is $I_{density}$, 5A/mm. The rms current through primary N_p is 1.479A in the example.

$$I_{PEAK} = 3.28A$$

 

$$I_{rms} = I_{PEAK} \times \frac{1}{\sqrt{3}} \times \sqrt{D}$$

$$= 3.46A \times \frac{1}{\sqrt{3}} \times \sqrt{0.62}$$

$$= 1.577A$$

The wire diameter f of N_p is 0.65mm.

$$I_{density}; 1mm^2 = I_{rms}; \pi \left(\frac{\Phi}{2} \right)^2$$

$$5A; 1mm^2 = 1.479A; \pi \left(\frac{\Phi}{2} \right)^2$$

$$\pi \left(\frac{\Phi}{2} \right)^2 = 0.295mm^2$$

$$\Phi \geq 0.613mm \Rightarrow 0.65mm$$

The rms current through secondary B_+ is 1.246A in the example.

$$I_{B-rms} = \sqrt{\frac{P_{B-OUT} \times 2 \times (N_{pmin} / N_{125V})^2}{L_m \times f_s - \min}} \times \frac{1}{\sqrt{3}} \times \sqrt{1-D}$$

$$= \sqrt{\frac{70W \times 2 \times 1.25^2}{554 \mu H \times 30kHz}} \times \frac{1}{\sqrt{3}} \times \sqrt{0.38}$$

$$= 1.291A$$

The wire diameter f of B_+ is 0.60mm.

$$5A; 1mm^2 = 1.291A; \pi \left(\frac{\Phi}{2} \right)^2$$

$$\pi \left(\frac{\Phi}{2} \right)^2 = 0.258mm^2$$

$$\Phi = 0.573mm$$

Calculated as above, the wire diameter f of 13V bias winding is 1mm.

References

1. Transformer and Inductor Design Handbook. 2nd ed. Col. Wm. T. McLyman. Marcel Dekker, Inc., 1988.
2. Flyback converter design using Fairchild Power Switch. Application note AN4105. Fairchild Electronics, 2000.

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.