

MEASURING low resistance

Simple low-resistance measurement usually relies on high direct current to produce a voltage drop, stressing the component under test. Reducing the current and amplifying the voltage drop can result in offset problems. Frantisek Michele explains the advantages of using ac to produce the drop.

Measuring resistors with low values can be tricky. The obvious method is to measure the voltage drop across the unknown resistor using a known current and then calculate its value.

Because the drop depends on the current through the resistor, the current needs to be large enough to produce a measurable voltage. For example, the voltage drop is only 10mV if the measured resistor is 0.1Ω and current through the resistor is 100mA.

Large currents supply large voltage drops. However, in many cases, the measured components will not tolerate such large currents. Also, the heat generated by within the component due to the large current can cause measurement errors.

This problem can be solved by amplifying the voltage drop so that less current is needed. If the amplifier has a 60dB gain, the output will be 0.1V if the current is 1mA and the resistor is still 0.1Ω.

The ac alternative

Operational amplifiers however have a dc input offset voltage. This offset causes an error when the input level is very low. An ac amplifier technique circumvents this problem.

Referring to Fig. 1, IC_A, C₁, and R₁₋₄ form a square waveform generator operating at around 300Hz. Diode D₁ limits the square wave to 6V peak-peak. Because the values of the measured resistor R_X and additional resistor R_A are much less than R₆, current through R_X will be,

$$I_X = 6/R_6 = 2 \text{ mA}$$

Then, IC_B's input is,

$$V_{IN} = I_X \times (R_X + R_A) = 0.002 \times (R_X + R_A)$$

Amplifier IC_B supplies the ac gain R₉/R₇=10. Diode D₂ with IC_C converts the ac signal to dc with gain of 1+R₁₁/R₁₀=10. DC amplifier

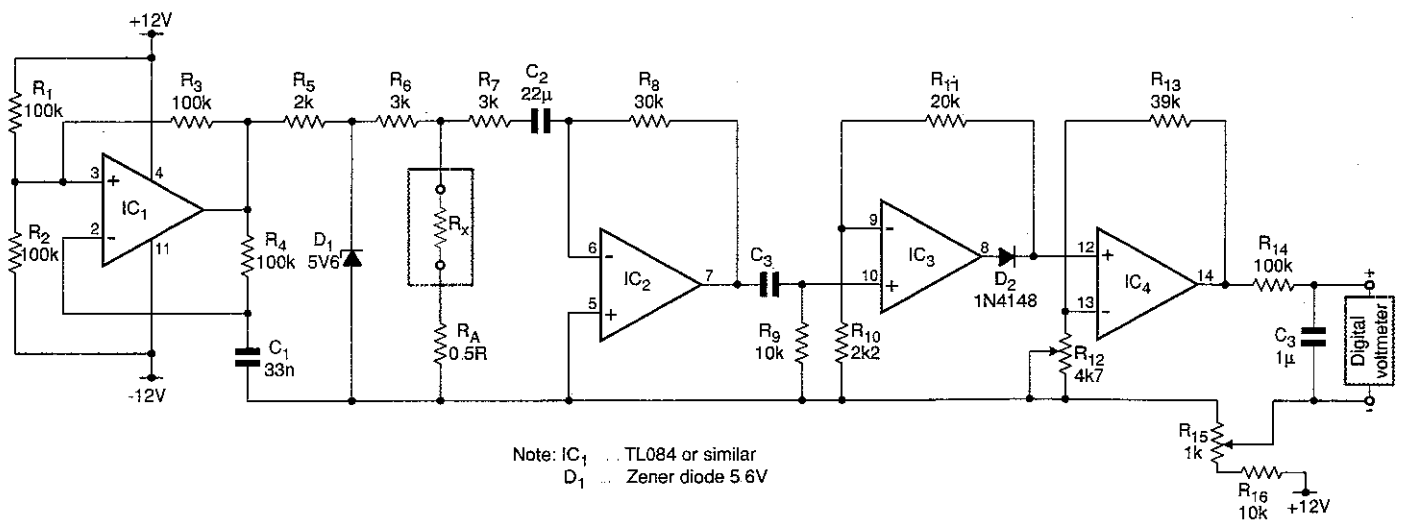


Fig. 1. Oscillator IC_A produces an ac voltage over the unknown resistor, which is then amplified, rectified and displayed. Since the stimulus is ac, high current and drift associated with dc schemes for measuring low resistance are removed.

V_D has a gain of $1+R_{13}/R_{12}$. As a result, the output is,

$$V_O = 0.5 \times V_{IN} \times 10 \times 10 \times (1 + R_{13}/R_{12}) = 0.1 \times (R_X + R_A) \times (1 + R_{13}/R_{12})$$

where 0.5 is the conversion efficiency for a 50% duty-cycle waveform. After the dc output is smoothed by R_{14} and C_4 , a digital voltmeter can measure R_X .

Resistor R_A supplies a base signal for the amplifiers. When $R_X=0$, R_A sends a 1mV peak-peak signal to IC_B . If $R_A=0$ and R_X is very small, IC_B 's noise may swamp the weak input. To compensate for the output offset due to R_A , R_{15} calibrates the digital voltmeter to zero when $R_X=0$. Adjusting R_{12} makes the scale $1\Omega/V$. Thus, a 2V digital voltmeter can measure resistances from 0.001 to 1.999 Ω .

Measure resistance of a capacitor

The equivalent series resistance, or esr, of a capacitor can be measured using Fig. 2.

Oscillator IC_1 forms a 50kHz square-wave generator. It drives a current waveform of about $\pm 180mA$ into the capacitor under test through R_1 and R_2 .

When R_3 is adjusted to the proper value, the voltage drop across the equivalent series resis-

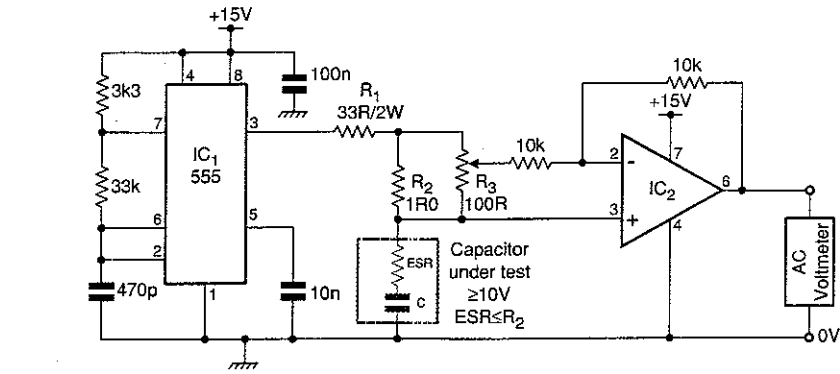


Fig. 2. Equivalent series resistance in a capacitor is particularly important in circuits such as switch-mode power supplies. Operating at 50kHz, this circuit drives about $\pm 180mA$ into the capacitor and looks at the resulting ac voltage over the 1Ω resistor via an op-amp.

tor is precisely nulled by the inverting amplifier IC_2 . Thus, V_O is the pure capacitor voltage which is the minimum voltage that can be produced at V_O .


To make an ac voltage measurement, adjust R_3 until V_O is minimised. Then note the position of the potentiometer and multiply it by the value of R_2 . That product equals the capacitor's esr.

The capacitor is biased about to 7.5V.


Lower-voltage capacitors cannot be measured with this circuit. Changing the value of R_2 allows other ranges of esr to be measured. However, for small R_2 values, the current level should be increased to keep a reasonable voltage across R_2 . This will require some sort of buffer.

The circuit is intended for capacitors greater than 100 μF . Ripple voltage becomes large for smaller values and accuracy decreases.

NEW & HARDLY USED TEST EQUIPMENT

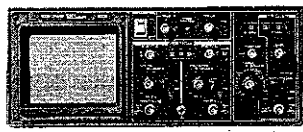

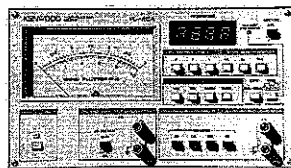
DUAL TRACE 20MHZ OSCILLOSCOPE MODEL HC3502
5MV - 20V/DIV; 0.2 μ Secs to 0.5Sec/DIV;
X - Y, X5 Magnifier; TV Sync etc
Used £180 Un-used £220



KENWOOD FL180A WOW/FLUTTER METER
0.003% - 10%; Frequency 3KHZ/3.15KHZ;
RMS/AVERAGE/PEAK; Weighted Filters; Digital Display
of rpm; 4 digit Frequency Counter (0.01KHZ-9.999KHZ;
55KHZ)
Used £400 Un-used £500



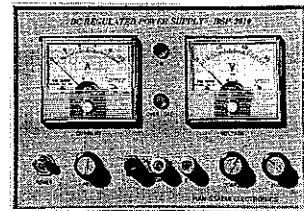PANASONIC VP8177A FM/AM SIGNAL GENERATOR
100KHZ-1.0MHZ; Output: -19dB to 99dB;
FM 0-100KHZ, AM 0-60%; 32 PreSet Memory; Digital
Display Frequency & Output
Used £450 Un-used £750



POWER SUPPLY MODEL HSP3010
0-30 Volts; 0-10Amps; Current Limiting; 2 metres
Used £235 Un-used £275



PANASONIC VP7637A STEREO SIGNAL GENERATOR
Generates Broadcast FM - RDS/ARI PreSet Memory; GP1B
Used £400 Un-used £700




GOODWILL GFC 80106 FREQUENCY COUNTER
Range 1HZ-120MHZ; 8
Digit Display;
15mVrms Sensitivity
Un-used £95



ANALOGUE MULTIMETER Model HC280TR
AC/DC Volts; DC Current
10 Amps; 17 Ranges
Continuity Buzzer;
Transistor Tester
Un-used £15



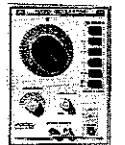GOODWILL GYT 427 DUAL CHANNEL AC MILLIVOLTMETER
10 μ V - 300V in 12
ranges; Frequency 10HZ-
1MHZ.
Used £100 Un-used £125



GOODWILL GAG 8088 AUDIO GENERATOR
Sine/Square 10HZ-1MHZ
in 5 ranges; 0.1% Low
Distortion; 5 steps Output
Attenuator.
Used £60 Un-used £80

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 7AS455 Dual Trace 100MHz Delay Cursors	£1190
TEKTRONIX 2445 4Ch. 100MHz Delay Cursors	£1500
PHILIPS PAC295 Dual Trace 350MHz Delay Cursors	£2900
N.P. 5200A Digitizing Oscilloscope 50MHz	£1100
TEKTRONIX 450 Dual Trace 550MHz Delay Sweep	£750
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep	£580
TEKTRONIX 485 Dual Trace 100MHz Delay Sweep	£460
TEKTRONIX 2215 Dual Trace 60MHz Delay Sweep	£360
PHILIPS 3655 2+1 Channel 50MHz Dual Trace Delay	£390
PHILIPS P43217 Dual Trace 50MHz Delay Sweep	£480
ORBIT GS11000 Duo Trace 30MHz	£290
ORBIT VS300 Duo Trace 20MHz (No handle)	£190
HYTRON 1210 Duo Trace 250MHz Memory Buffer	£790
HYTRON 458 Duo Trace 100MHz Delay Sweep Dig Storage	£730
HYTRON VCS45 Duo Trace 100MHz Delay Storage	£1000
HYTRON VCS41 Duo Trace 40MHz Dig Storage	£650
RESCORP 5952 Dual Trace 200MHz Dig Storage Plotter Output	£650
N.P. 1741A Dual Trace 100MHz Analogue Storage	£460
TEKTRONIX 466 Dual Trace 100MHz Delay Sweep Analogue Storage	£460
TEKTRONIX 434 Dual Trace 20MHz Analogue Storage	£320
LEADER LS1040 10MHz/Scope 200MHz Dig Storage LCD Display	£300

THIS IS JUST A SAMPLE, MANY OTHERS AVAILABLE

N.P. 8520C Sweep Osc with 8620B 2-18.6GHz	£2000
N.P. 8520C Sweep Osc with 8622B 7.01-2.4GHz	£2000
N.P. 8550A Syn Sig Gen 0.1-2.1MHz	£1750
MARCONI 2219 Synthesised AM/FM Sig Gen 800KHz-1940Hz	£1150
MARCONI 2222 AM/FM Sig Gen 100KHz-15Hz	£1000
MARCONI 2118A Synthesised AM/FM Sig Gen 800KHz-520MHz	£1000
N.P. 8542A AM/FM Sig Gen 500KHz-1MHz	£900
N.P. 8520C Spectralator Main Frame only	£300
FARNELL SS2520 Synthesised AM/FM Sig Gen 10-520MHz	£480
FARNELL TR3200 Transmitter Test Set	£460
WATELEC 2000 AM/FM Sig Gen 1-300MHz Synthesised	£225
MARCONI 17015 AM/FM Sig Gen 10-320MHz	£150
N.P. 8515A UHF Signal Generator 1.8-4.5GHz	£300
N.P. 8514A UHF Signal Generator 500MHz-2.4GHz	£300
MARCONI TR2311A Distortion Factor Meter 20Hz-200MHz 0.05% De-embed	£225
MARCONI TR3531 Audio Power Meter 50W	£250
N.A.S. Video Meter UFS2 with UFS2C 40Hz-100MHz	£1500
WILTRON 6410A Programmable Sweep Gen 1-2GHz	£1500
N.P. 3338B Synthesised Lev Gen 10Hz-21MHz	£800
N.P. 8150A Programmable Pulse Gen 50MHz	£1250
MARCONI 2325 Modulation Meter	£2250
PHILIPS PM5134 Sweep Fun Gen 0.001Hz-20MHz Sine/Sw/Tri etc	£500
N.P. 5006 Signature Analyser	£150
N.P. 5004A Signature Analyser	£100
N.P. 5450B Attenuator DC-18GHz 10dB in 10dB steps	£350
N.P. 5451A Wave Analyser 15Hz-50MHz LED Readout	£300
N.P. 8495A Vector Voltmeter 1-100MHz	£200
N.P. 8115A Programmable 50MHz Pulse Generator	£200
PHILIPS PM 5134 Sweep Fun Gen 0.0001 MHz-20MHz Sine/Sw/Tri/Pulse	£500
N.P. 3317A Fun Gen 0.1Hz-13MHz AM/FM Sweep/Freq/Gate etc	£480
N.P. 8494B with 8495A Attenuators Opt 0dB and 10/17/13A	£1750
Metrohm/Octavia Drive	
TEKTRONIX 760 Stereo Audio Monitor	£2750
BRUNNIT Off Air Standard type 2A-01	£900
BRUNNIT Series 808 Electric Power/Download Analyser	£200
BRUNNIT Universal Disturbance Analyser Series 526A	£
AVP Breakdown AC/DC and Isolation Tester RM215/2	£480
PHILIPS PM5519 Colour Pattern Generator	£460
N.P. 5432A Converter 740Hz 1MHz	£250
N.P. 5340A Counters 10Hz-15GHz	£1750

Used Equipment - GUARANTEED. Manuals supplied if possible.
This is a VERY SMALL SAMPLE OF STOCK, SAE or Telephone for lists. Please check availability before ordering.
CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS. RG6 1PL
Telephone: (0118) 9268041. Fax: (0118) 9351696
Callers Welcome 9am-5.30pm Monday to Friday (other times by arrangement)

BRUEL & KJØER EQUIPMENT AVAILABLE PLEASE ENQUIRE

SPECTRUM ANALYSERS

N.P. 8556A 0.01-225Hz	£3500
ALITECH 727 0.001-20GHz	£2000
N.P. 8554 with 8558B 100kHz-1500MHz	£2750
N.P. 112 with 8558B 100kHz-1500MHz	£1500
MARCONI TR7270 30Hz-110MHz	£700
MARCONI 2370 with TR2373 30Hz-1.25GHz	£1750
MARCONI 2382 100Hz-400MHz	£4800
N.P. 1352A Dual Channel 500Hz	£2000

Some N.P. 1417 Systems Available - Please enquire